
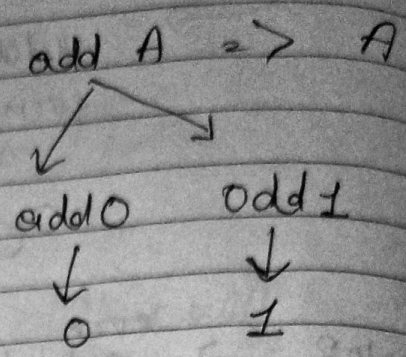


A O A O A O A

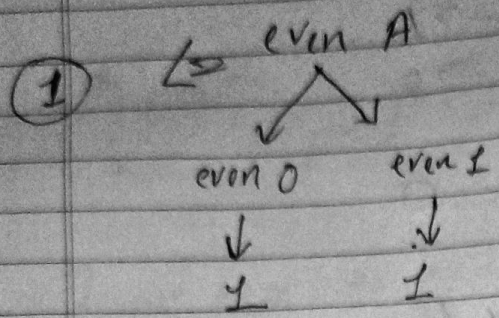



\* NAND and NOR as universal gates

NAND as universal gates

• NOT gate using NAND

NAND gate



NOT

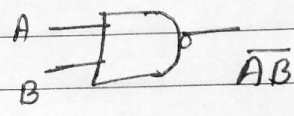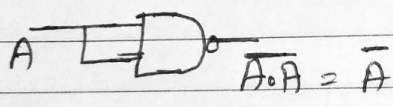


1 NAND gate is required for NOT gate

• AND

NAND

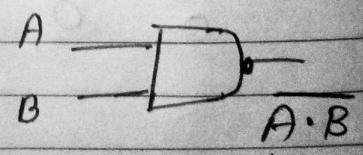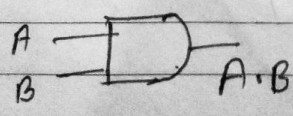


## • AND using NAND

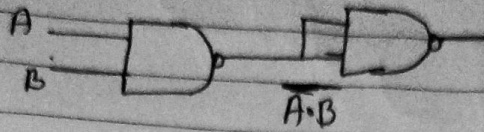



$$\overline{\overline{A \cdot B}} \Rightarrow A \cdot B$$

2 NAND gate is used

## • OR gate

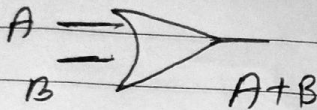



NAND

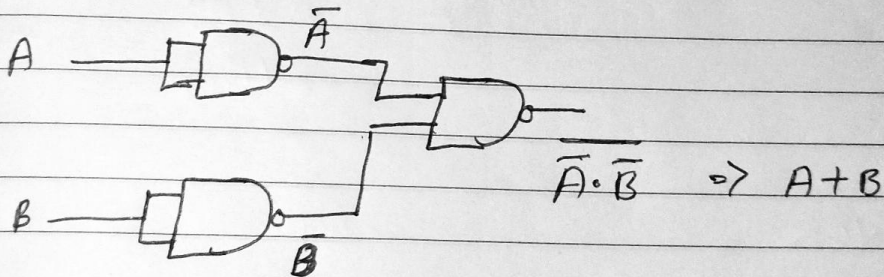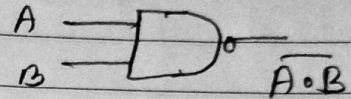


3 NAND gate is used

## \* NOR gate

NAND gate

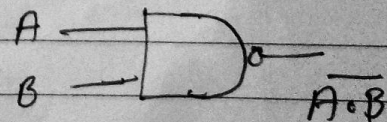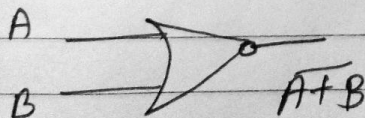


## NOR gate using NAND

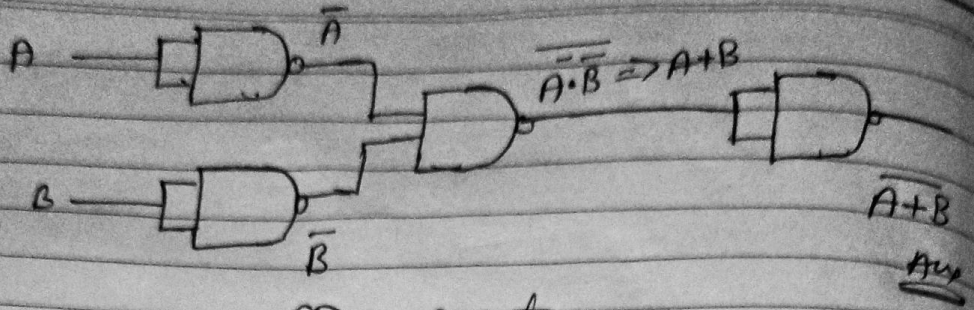

④ NAND gates

## • XOR

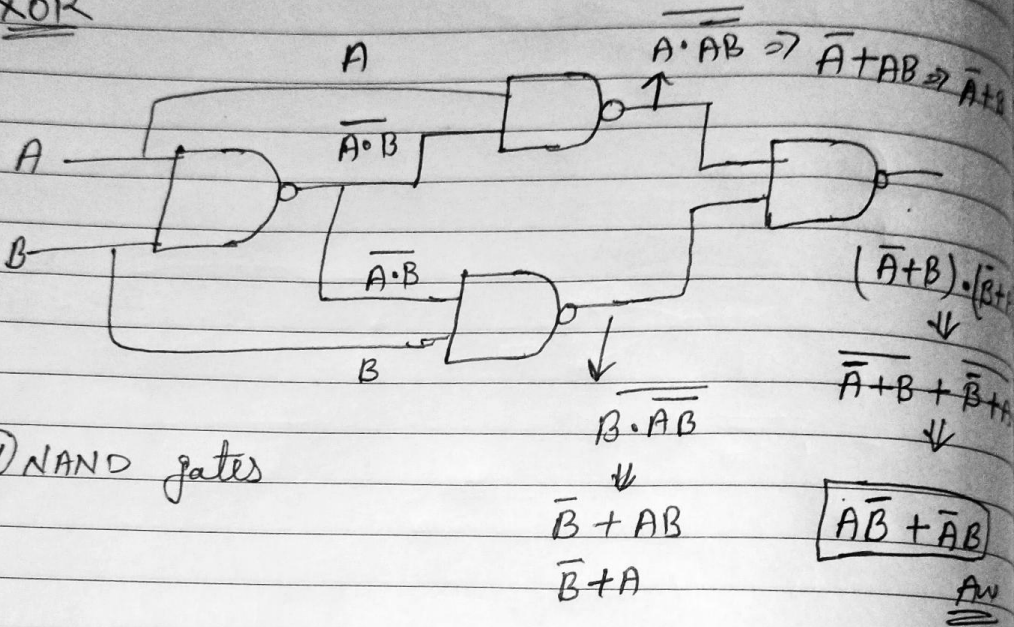

④ NAND gates

## • XNOR

Make XOR and add one NAND gate in the end




	<u>NAND</u>
NOT	1
AND	2
OR	3
NAND	1
NOR	4 [3+1]
XOR	4
XNOR	4+1 = 5

NOR


1
3
2
4
1
5
4

\* NOR as universal gate


1 NOT gate

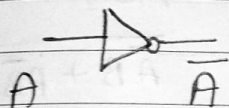

NOR gate

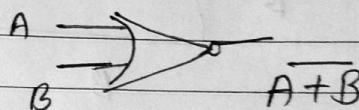

NOT gate using NOR

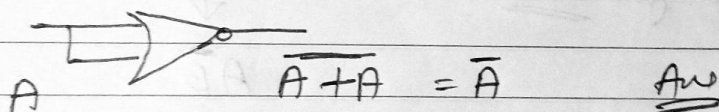


① NOR gate used

2 OR gate




OR gate using NOR

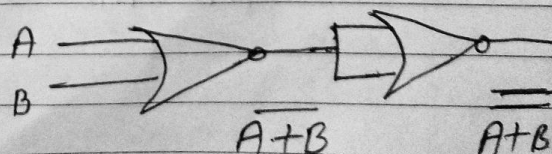


② NOR used

AND NOR gate

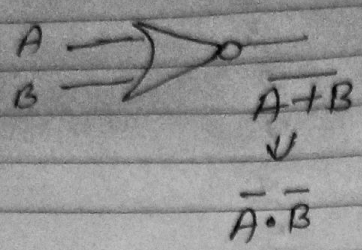


AND gate using NOR

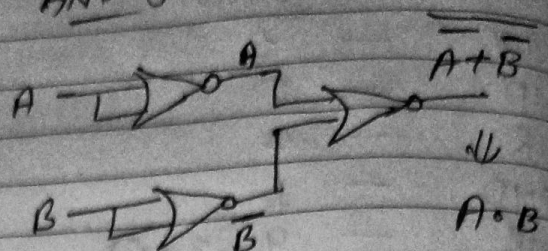

③ NOR gate used

XNOR

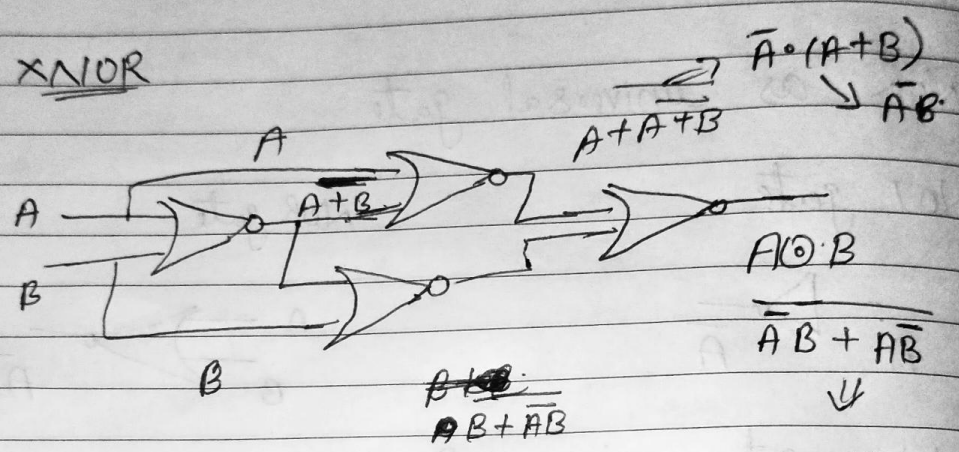

④ NOR gate used

XOR

$$\overline{A}B + A\overline{B}$$

$\downarrow$

XNOR

$$AB + \overline{A}\overline{B}$$

$\Rightarrow$

Proof

$$\overline{A}B \cdot \overline{A}\overline{B} \Rightarrow (A + \overline{B}) \cdot (\overline{A} + B)$$

$$AB + \overline{A}\overline{B}$$

Ans

XNOR

$$AB + \bar{A}\bar{B} \Rightarrow \bar{A}B + A\bar{B}$$


XORProof : ↓

$$AB \cdot \bar{A}\bar{B} \Rightarrow (\bar{A} + B) \cdot (A + \bar{B})$$

$$\bar{A}B + A\bar{B}$$

AnsXOR

\* Make ~~XNOR~~ and add "one" NOR in the end

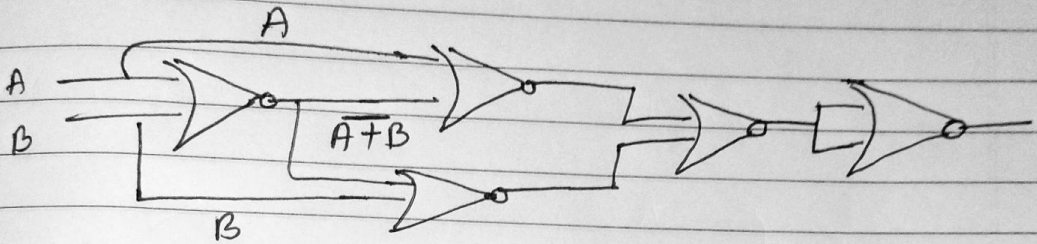⑤ NOR gate used

\* Principal of duality

$$+ \rightarrow \cdot$$

$$\cdot \rightarrow +$$

$$1 \rightarrow 0$$

$$0 \rightarrow 1$$

$$OR \rightarrow AND$$

$$AND \rightarrow OR$$

$$NAND \rightarrow NOR$$

$$NOR \rightarrow NAND$$

They are  
dual of  
each other

$$XOR \rightarrow XNOR$$

$$XNOR \rightarrow XOR$$

$$NOR \rightarrow NOT$$

NOT is self


dual



$$A + \bar{A} = 1 \rightarrow \text{Tautology}$$

$$A \cdot \bar{A} = 0 \rightarrow \text{Tautology}$$

Expression is ~~not~~ tautology iff its dual is tautology

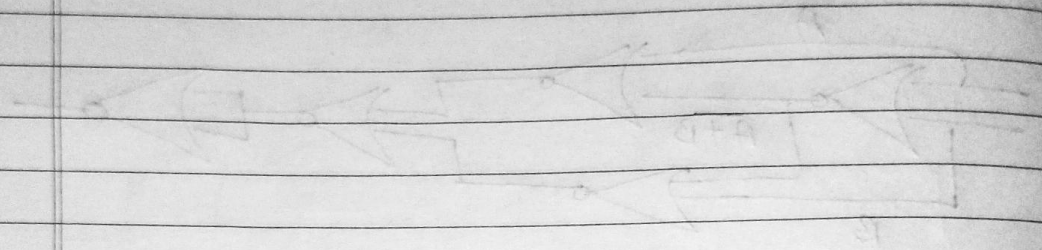

Example 1: (A + B) \* A

Truth Table of (A + B) \* A

A	B	(A + B) * A
0	0	0
0	1	0
1	0	1
1	1	1