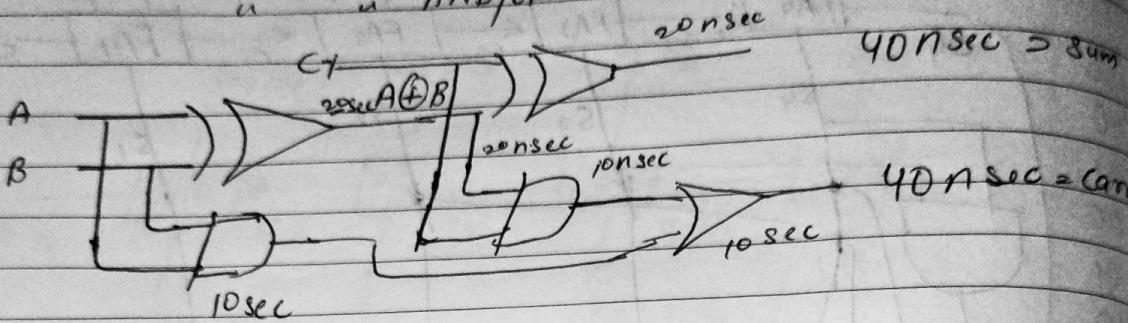


Look ahead carry

L-26


- * Consider an implementation of F.A using 2 MA

→ delay of XOR — 20 nsec
 " " AND/OR — 10 nsec



Total delay 40 sec

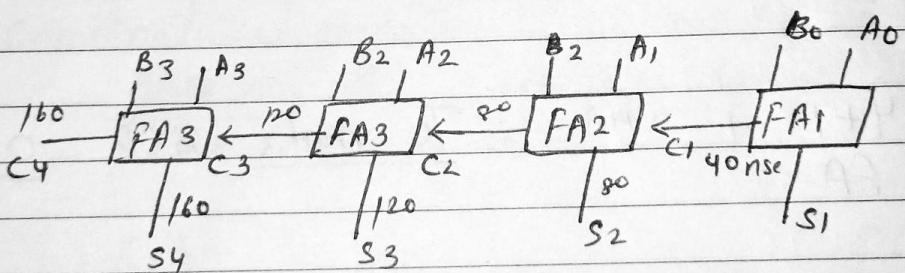- * 4 bit parallel adder — Total delay?
 — 1 FA $\rightarrow 40 \text{ nsec}$



160 nsec


$\frac{1}{n} \text{ FA delay} = m \times n$

2 bit parallel adder implemented using
2 HA

XOR - 20 nsec

AND/OR - 10 nsec

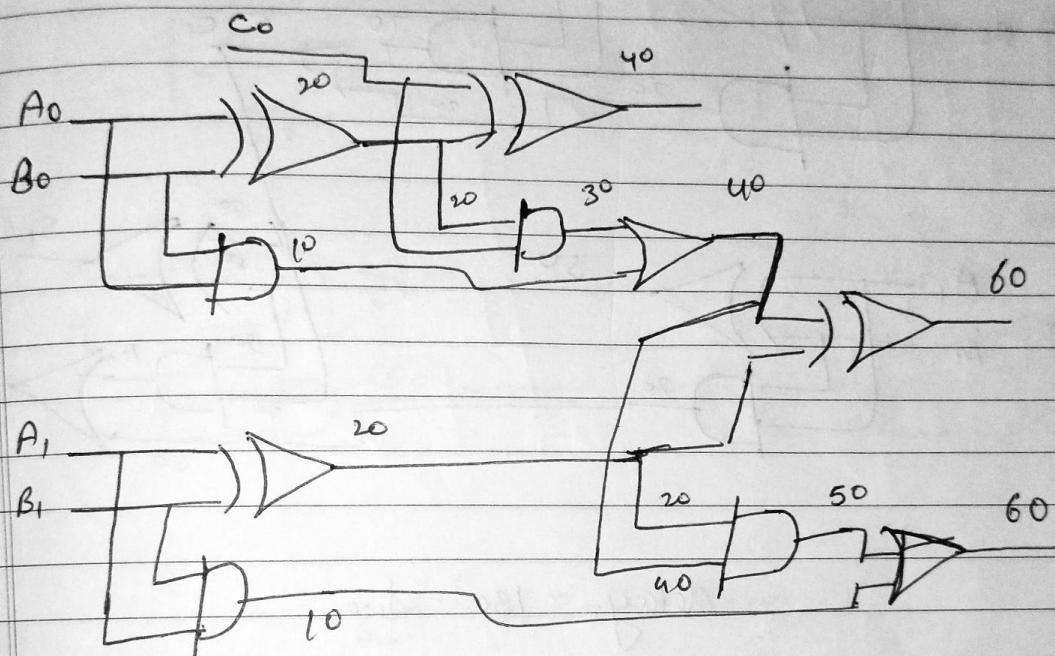
$$\begin{matrix} & \text{FA} \\ n_1 = & \begin{bmatrix} e_1 & c_0 \\ A_1 & A_0 \\ B_1 & B_0 \\ c_2 & S_1 & S_0 \end{bmatrix} \text{FA} \\ n_2 = & \end{matrix} = 2 \text{ FA} \Rightarrow 4 \text{ HA}$$



Total delay 60 nsec

α bit parallel adder \rightarrow delay?




HA

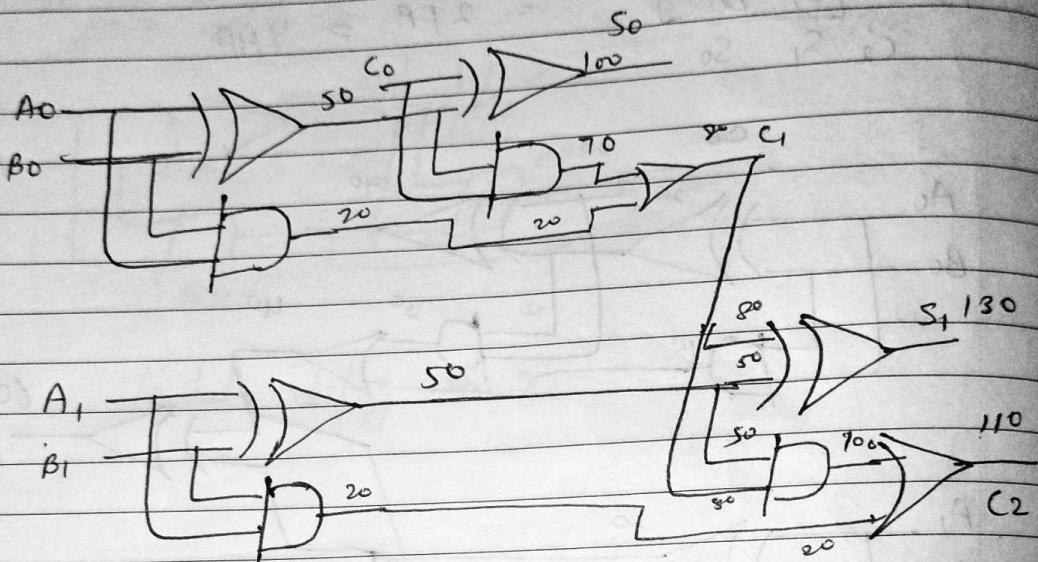XOR \rightarrow 50 nsecAND \rightarrow 20 "OR \rightarrow 10 " $c_1 \ c_0$ $n_1 \rightarrow A_1 \ A_0$ $n_2 \rightarrow \underline{B_1} \ B_0$ $(c_2 \ S_1 \ S_0)$ 

delay ≈ 130 nsec

2bit parallel adder
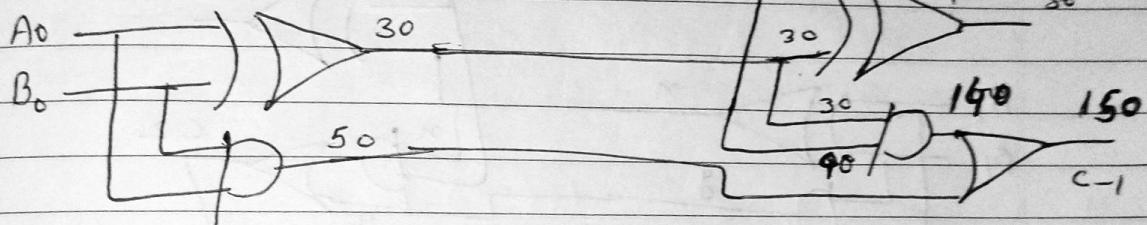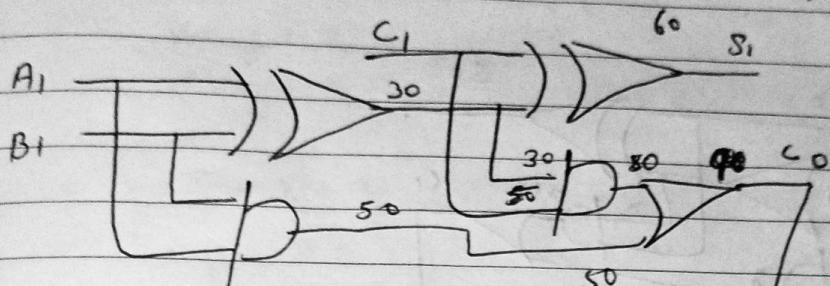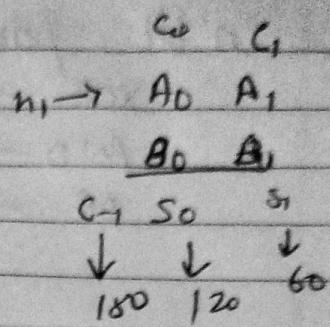
$$\begin{array}{l} \text{HA} \\ \text{XOR} - 30 \\ \text{AND} - 50 \\ \text{OR} - 10 \end{array}$$



$$\text{delay} = 150 \text{ ns}$$

~~n-bit parallel adder~~


~~n XOR - n only HA~~

~~AND - y~~

~~OR - z~~

✓ The Good Paper

| | | | |
|-------|-------|-------|-------|
| c_2 | c_1 | c_0 | s_4 |
| A_3 | A_2 | A_1 | B_0 |
| B_3 | B_2 | B_1 | B_0 |
| c_4 | s_3 | s_2 | s_1 |

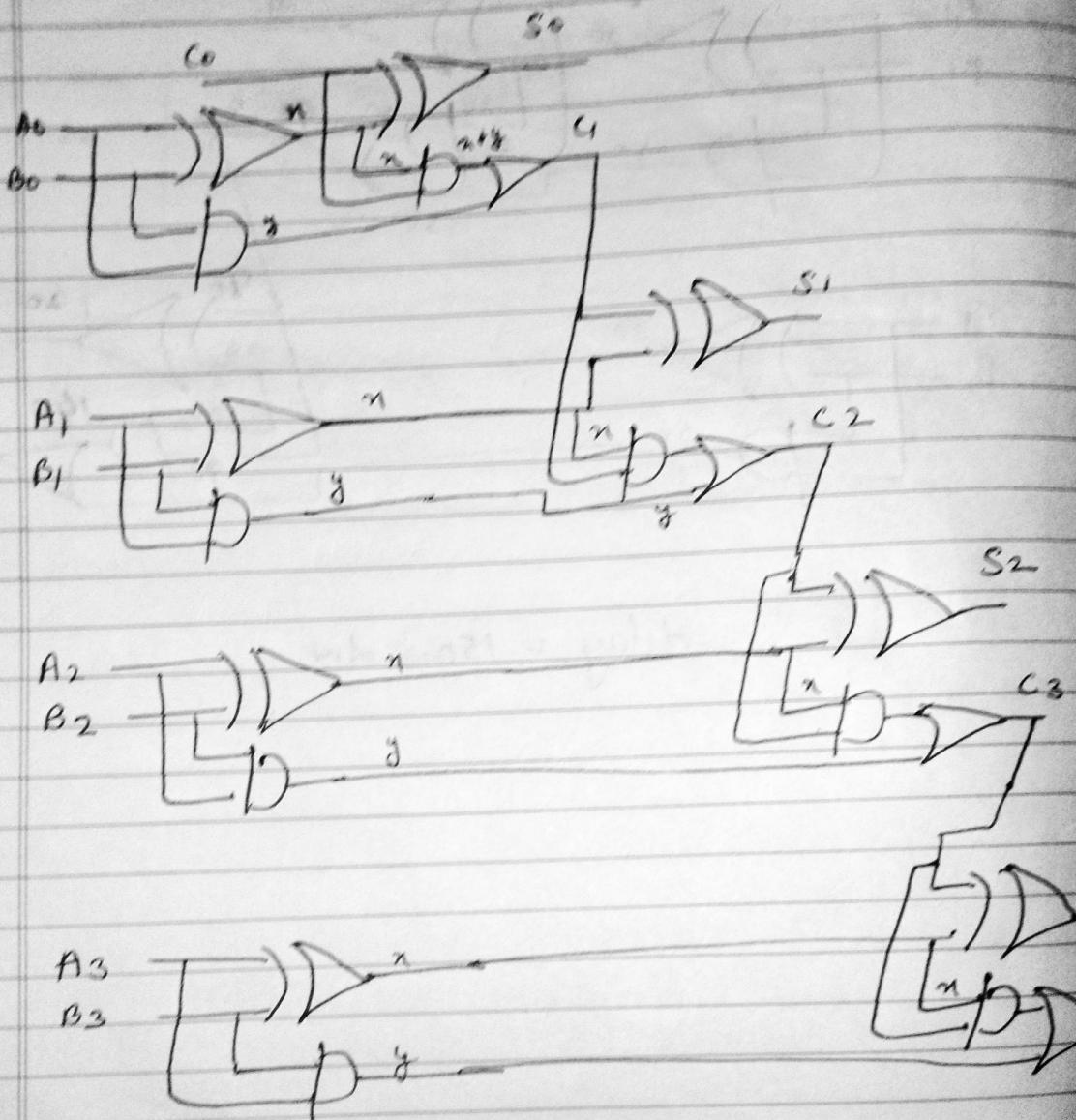

$$\begin{aligned}
 S_0 &= 2n \\
 C_1 &= n+y+z \\
 S_1 &= n+y+z+n \\
 C_2 &= n+y+z+y+z \\
 S_2 &= n+y+z+y+z+n \\
 C_3 &= n+y+z+y+z+y+z \\
 S_3 &\rightarrow n+y+z+y+z+y+z+n \\
 C_4 &\rightarrow n+y+z+y+z+y+z+y+z
 \end{aligned}$$

$\frac{\text{Ans}}{2}$

$$\begin{aligned}
 S_0 &= 2n \\
 C_1 &= n+y+z
 \end{aligned}$$

$$\begin{aligned}
 \text{Total delay} &= S = 2n(n-1)^*(y+z) \\
 C &= n+y+z(n-1)^*(y+z)
 \end{aligned}$$

Formula for n bit parallel adder
only using H.o.A

Total delay of n bit parallel adder if it is implemented using H.o.A only
delay of XOR - n , AND - y and OR - z


$$\begin{aligned}
 \text{Sum} &= 2n(n-1)(y+z) \\
 \text{Carry} &= n+y+z(n-1)(y+z)
 \end{aligned}$$

$$\text{Sum} = 2n + (n-1)(y+z) \Rightarrow n + \boxed{n + (n-1)(y+z)}$$

$$\text{Carry} = n+y+z(n-1)(y+z) \Rightarrow n + \boxed{(y+z)(n-1)(y+z)} \text{ diff}$$

if $n > y+z$, sum will decide
the total delay

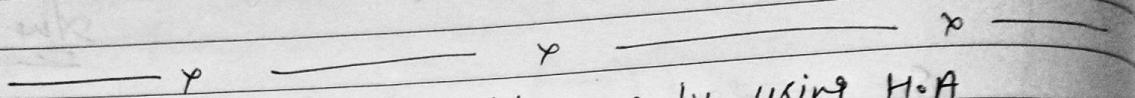else if $y+z > n$, carry will decide
the total delay
else "any of them"



4 bit parallel adder only using H.A
 $\text{XOR} - 50, \text{AND} - 30, \text{OR} = 20$

$$\begin{aligned}\text{Sum} &= 2n + (n-1)(y+z) \\ &= 100 + 3 \times 50 \\ &= 250 \text{ nsec}\end{aligned}$$

$$\begin{aligned}\text{Carry} &= n+y+z+(n-1)(y+z) \\ &= 50+20+30+3 \times 50 \\ &= 250 \text{ nsec}\end{aligned}$$



8 bit parallel adder

Date: _____
Page No.: _____

$\text{XOR} \rightarrow 20$, $\text{AND} \rightarrow 50$, $\text{OR} \rightarrow 10$


$$\begin{aligned}\text{Sum} &= 2^n (n-1) (y+z) \\ 40 &+ 7 \times 60 = 460\end{aligned}$$

$$\begin{aligned}\text{Carry} &= n+y+z (n-1)(y+z) \\ 80 &+ 7 \times 60 = 500 \quad \underline{\underline{\text{Ans}}}\end{aligned}$$



Total delay $\rightarrow 500$

Same

ans without using formula c_1, c_0

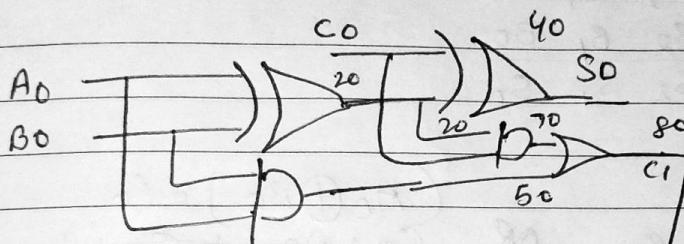
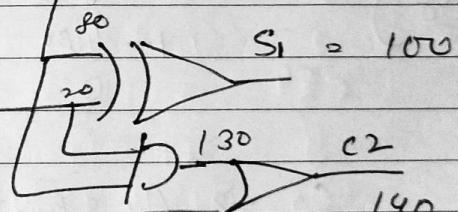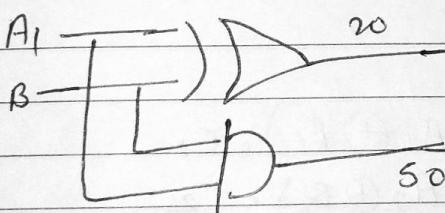
$$\begin{aligned}n_1 - A_1, A_0 \\ n_2 - B_1, B_0 \\ C_2, S_1, S_0\end{aligned}$$



$$\begin{aligned}S_0 &= 40 \\ C_1 &= 80\end{aligned}$$

$$\begin{aligned}S_1 &= 100 \\ C_2 &= 140\end{aligned}$$

$$\begin{aligned}S_0 &\rightarrow 40 * 60 \times 7 = 460 \\ C & 80 * 60 \times 7 = 500\end{aligned}$$

~~Ans~~