

L-16

* Logic gates

gate \rightarrow It will allow or does not allow current to pass through it.

It is used to implement logic function using gates


* Types

\hookrightarrow Basic / fundamental	\hookrightarrow derived
\hookrightarrow NOT	\hookrightarrow NAND
\hookrightarrow AND	\hookrightarrow NOR
\hookrightarrow OR	\hookrightarrow XOR
	\hookrightarrow XNOR

* AND gate

① n inputs and only '1' output

② symbol

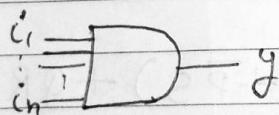

$$y = i_1 \cdot i_2 \cdot \dots \cdot i_n$$


③ output of AND gate is '1' if all inputs are '1'

OR


if atleast one input is '0' then out will be 0

4 Truth table

A	B	$A \cdot B$	$f(A, B) = A \cdot B$
0	0	0	
0	1	0	
1	0	0	
1	1	1	

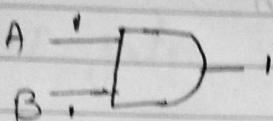5 Circuit diagram

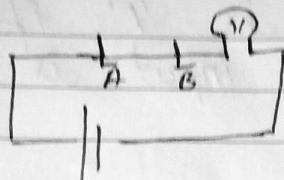1 → Presence of current
0 → Absence of current



An AND gate AKA Series circuit

6 How many minterms


Q → Consider AND function of 'n' boolean variables how many minterms will be present

Ans One minterm

• OR function/gate

① n I/P & O/P is 1

② symbol

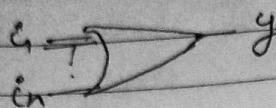

$$y = \bar{y}_1 + \bar{y}_2 + \bar{y}_3 + \dots + \bar{y}_n$$

③ output of OR gate is '1' iff at least one of its input is 1

④ Truth Table

A	B	$A+B$
0	0	0
1	0	1
0	1	1
1	1	1

$$f(A, B) = (A+B)$$


$$\bar{A}B + A\bar{B} + AB$$

$$B + \bar{B}A$$

↙ Absorption law

$$A+B$$

⑤ circuit diagram

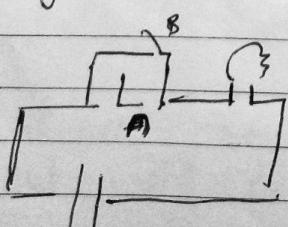

OR aka parallel circuit

6 How many minterms


\downarrow n var OR function
 2^n $2^n - 1$ Ans

minterms

* NOT gate

① 1 I/P and 1 O/P


② Symbol

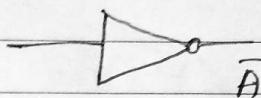

③ output not gate is '1' if input '0'

④	A	\bar{A}	$f(A) = \bar{A}$
	0	1	
	1	0	


⑤ circuit diagram

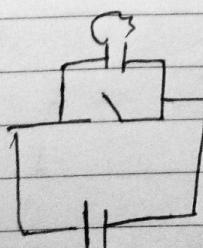

6 How many minterms
→ Only one


* NAND gate

↳ Bubbled AND gate
Not

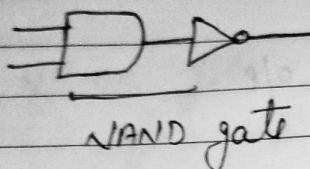

1) n inputs and one output


2) Symbol

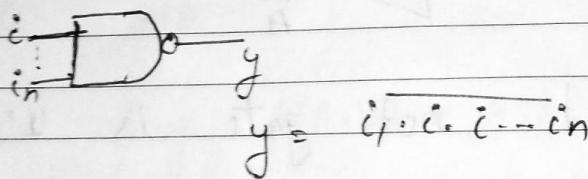

③ output of NAND gate '1' if atleast one of its input is '0'

④ Truth Table

A	B	y
0	0	1
0	1	1
1	0	1
1	1	0

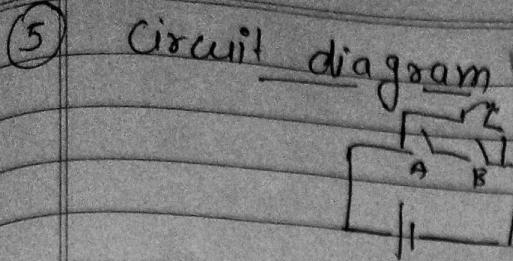


⑥ No of minterms

$$2^n - 1 \quad \underline{\text{Any}}$$


* NOR gate

↳ Bubble OR gate

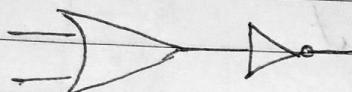

① n IP and 'Y' output

② symbol

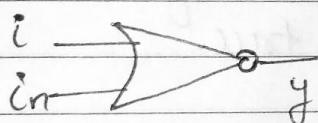

$$y = \overline{i_1 + i_2 + i_3 + \dots + i_n}$$

③ output of nor gate is 'Y' if all the inputs are '0'

④ Truth table

$$A \ B \quad Y \Rightarrow A + B$$

$$0 \ 0 \quad 1$$


$$0 \ 1 \quad 0$$

$$1 \ 0 \quad 0$$

A	B	Y
1	1	0
0	1	1
1	0	1
0	0	1


No. of minterms $\Rightarrow 1$

⑤ circuit diagram

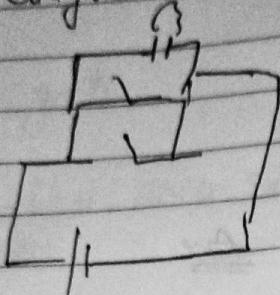

* XOR

① n input & 1 output

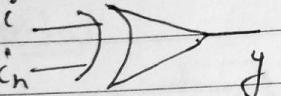②  $y = i_1 \oplus i_2 \oplus i_3 \dots$

③ o/p of XOR is 1 iff odd of literals (variables) are true.


④ Truth Table

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Minterms $\Rightarrow \bar{A}B + A\bar{B}$

A	B	C	$f(A, B, C)$	$\bar{A}\bar{B}C + \bar{A}B\bar{C}$
0	0	0	0	$+ A\bar{B}\bar{C} + ABC$
0	0	1	1	
0	1	0	1	
0	1	1	0	
1	0	0	1	
1	0	1	0	
0	1	1	0	
1	1	1	1	

5 Circuit diagram

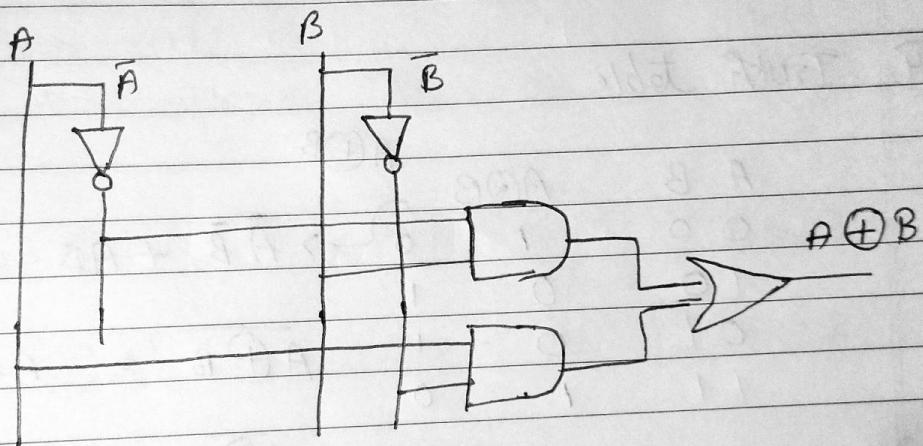

6 How many minterms

$$\frac{2^n}{2} \rightarrow \frac{2^n}{2} \rightarrow 2^{n-1}$$


Diagram illustrating the calculation of the number of minterms:

- Start with 2^n (indicated by a downward arrow).
- Divide by 2 (indicated by a downward arrow).
- Divide by 2 again (indicated by a downward arrow).
- The result is 2^{n-1} .

* XNOR gate

① input n, 8 o/p 1

② symbol

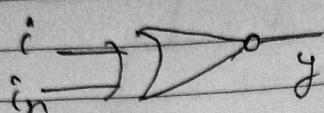

$$y = i_1 \oplus i_2 \oplus i_3 \dots$$

③ o/p of XNOR is 1 iff even no. of literals are false

④ Truth Table

A	B	$A \oplus B$	$A \oplus B$
0	0	1	$\rightarrow \bar{A}\bar{B} + A\bar{B}$
1	0	1	
0	1	1	$\bar{A} \oplus B = A \cdot B$
1	1	0	

$$\bar{A} \oplus B = A \oplus B$$

A	B	C	$A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
0	1	1	0
1	1	1	1

$$101_2 = 0$$

If we've fn of even var then XOR and XNOR are opposite of each other

If we've fn of odd var then XOR and XNOR are same

		XOR	XNOR
A	B	$A \oplus B$	$A \odot B$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

XOR \rightarrow diff
 XNOR \rightarrow similarities

$$A' \oplus B \Leftrightarrow A \odot B \quad | \quad A \oplus B = A\bar{B} + \bar{A}B$$

$$A \oplus B' \Leftrightarrow A \odot B \quad | \quad \bar{A}\bar{B} + AB$$

$$A' \oplus B' \Leftrightarrow A \oplus B$$

$$A' \odot B = A \oplus B$$


$$A \odot B' = A \oplus B$$

$$A' \odot B' = A \odot B$$

$$\overline{\overline{XOR}} \quad 1 \oplus 1 \oplus 1 \oplus 1 \oplus 1 \dots = 0_{An} \quad ① \rightarrow \text{even times}$$

$$1 \oplus 1 \oplus 1 \oplus 1 \oplus 1 \dots = 1_{An} \quad ② \rightarrow \text{odd times}$$

gate question

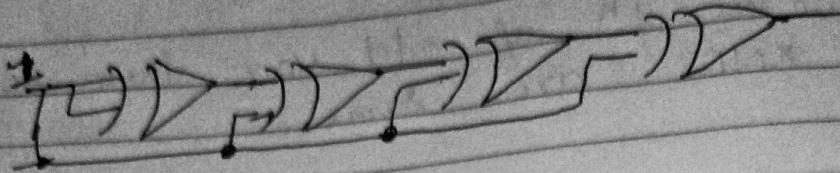

if we have 20 XOR gates output will be ?

$$1 \oplus 1 \oplus 1 \oplus 1 \oplus 1 \dots \text{ Ans} \rightarrow 1$$

We have 20 XOR gate so no. of '1's will be '21' and '21' is odd so ans is '1'

$$\begin{array}{ccccccc} 0 & \oplus & 0 & \oplus & 0 & \oplus & 0 \\ \checkmark & & \diagup & & \diagdown & & \\ 0 & & 0 & & 0 & & 0 \end{array} \rightarrow \begin{array}{l} \text{odd } 0's \\ \text{even } 0's \end{array}$$

Ans will 0 only

XOR XNOR

$$1 0 1 0 1 0 1 \dots \rightarrow \text{odd } 1$$

$$\begin{array}{ccccccc} \checkmark & 1 & 1 & 1 & 1 & 1 & 1 \\ \diagup & \diagdown & \diagup & \diagdown & \diagup & \diagdown & \diagup \\ 1 & 1 & 1 & 1 & 1 & 1 & 1 \end{array} \rightarrow \begin{array}{l} \text{odd } 1 \\ \text{even } 1 \end{array}$$

$$0 0 0 0 0 0 \dots \rightarrow \text{odd } 0's \Rightarrow 0$$

$$\begin{array}{ccccccc} \checkmark & 1 & 1 & 1 & 1 & 1 & 1 \\ \diagup & \diagdown & \diagup & \diagdown & \diagup & \diagdown & \diagup \\ 1 & 0 & 1 & 0 & 1 & 0 & 1 \end{array} \rightarrow \begin{array}{l} \text{odd } 1 \\ \text{even } 1 \end{array} \Rightarrow 1$$

$\text{XOR} \rightarrow \text{odd literal true}$

odd 1's $\rightarrow 1$

even 1's $\rightarrow 0$

$$Q \leftarrow \begin{cases} \text{even} \\ \text{odd} \end{cases} = 0$$

$\text{XNOR} \rightarrow \begin{cases} \text{even} \\ \text{odd} \end{cases} \text{ literal false}$

$$1 \xrightarrow{\text{odd}} \begin{cases} \text{even} \\ \text{odd} \end{cases} J = 1$$


$$Q - \text{odd} = 0$$

$$\text{even} = 1$$

$$1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 \oplus 1 \Rightarrow 5$$

$$100 \oplus 100 \oplus 101 \oplus 0101 \oplus 0001 \Rightarrow 0$$

$$A \oplus A \oplus A \oplus A \dots$$

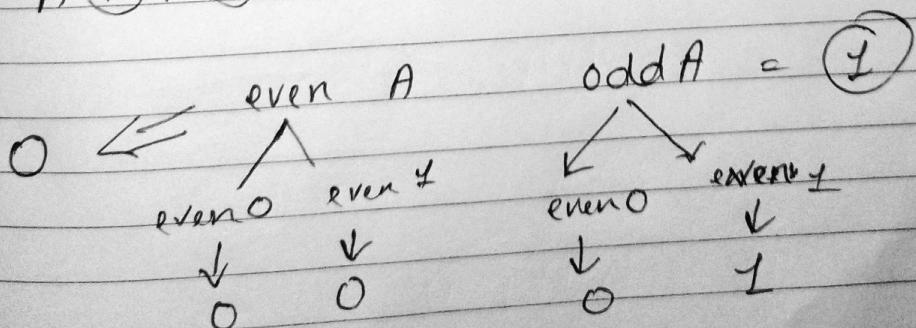

AOAOAOA

①

even A

even 0 even 1
↓ ↓
0 1

add A \Rightarrow A

add 0 odd 1
↓ ↓
0 1